

Chapter 7 :: Microarchitecture

Digital Design and Computer Architecture

Copyright © 2007/2013 Elsevier

David Money Harris and Sarah L. Harris

Lectured by Jeong-Gun Lee

School of Software, Hallym University



CPU 만들기

나만의

MIPS processor → Verilog HDL → 회로

[*HDL?
Hardware Description Language]

다운로드


이런저런

흥건동

Hallya ...

* MIPS 프로세서 설계 및 구현
- FPGA 이용

완전
백신!

 


Chapter 7 :: Topics

- **Introduction**
- **Performance Analysis (성능 분석)**
- **Single-Cycle Processor (단 사이클 프로세서)**
- Multicycle Processor
- Pipelined Processor
- Exceptions
- Advanced Microarchitecture



Introduction

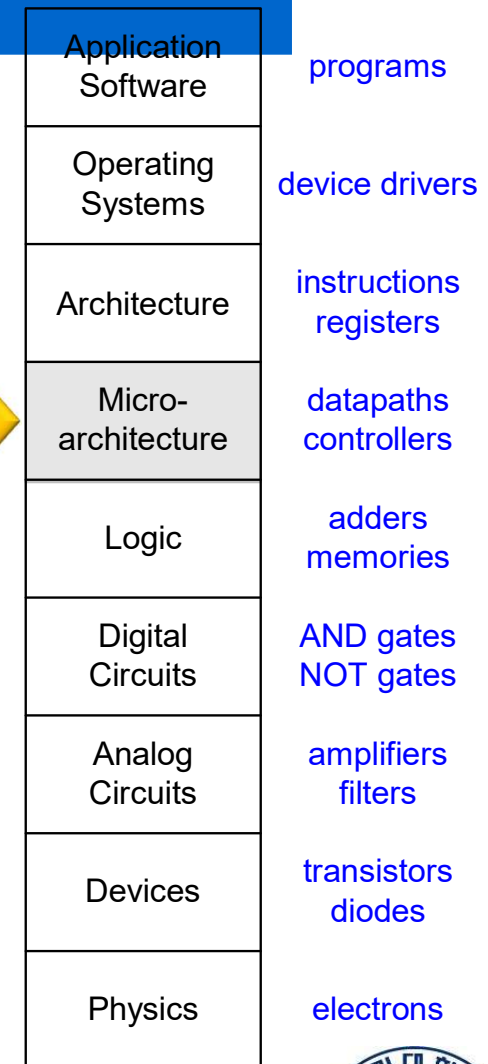- Microarchitecture: how to implement an architecture in hardware
(마이크로아키텍처: 아키텍처를 어떻게 하드웨어로 구현할 것인가!!!)
- Processor:
 - Datapath: functional blocks
(데이터패스: 기능 블록)
 - Control: control signals
(제어: 제어신호)
- 아키텍처 ? → 명령어 집합



Microarchitecture

- Multiple implementations for a single architecture:
- (하나의 아키텍처에 여러 개의 구현 방법!)
 - Single-cycle (단일 사이클)
 - Each instruction executes in a **single cycle**
 - Multicycle (다수 사이클)
 - Each instruction is broken up into a series of shorter steps
 - Pipelined (파이프라인)
 - Each instruction is broken up into a series of steps
 - Multiple instructions execute at once.



Processor Performance

- Program execution time (프로그램 수행시간)

$$\text{Execution Time} = (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

- Definitions(정의):
 - $\text{Cycles/instruction} = \text{CPI}$ // 명령어당 요구되는 클럭 사이클
 - $\text{Seconds/cycle} = \text{clock period}$
 - $1/\text{CPI} = \text{Instructions/cycle} = \text{IPC}$ // 한클럭당 수행되는 명령어수
- Challenge is to satisfy constraints of:
- (도전은 다음 제약사항들을 만족시키는 것)
 - Cost (비용)
 - Power (파워 소모)
 - Performance (성능)



Clock Cycle ?



MIPS Processor

- We consider a subset of MIPS instructions:
 - R-type instructions: **and, or, add, sub, slt**
 - Memory instructions: **lw, sw**
 - Branch instructions: **beq**

+ addi, bne, j, jr, jal

* Architecture < 아키텍처 >

⇒ 명령어 집합

→ { and, or, add, sub, slt, lw, sw, beq... }




Architectural State (아키텍처 상태)

- Determines everything about a processor:
프로세서에 대한 모든 것을 결정하자!
 - PC
 - 32 registers
 - Memory



MIPS State Elements (상태 요소들)

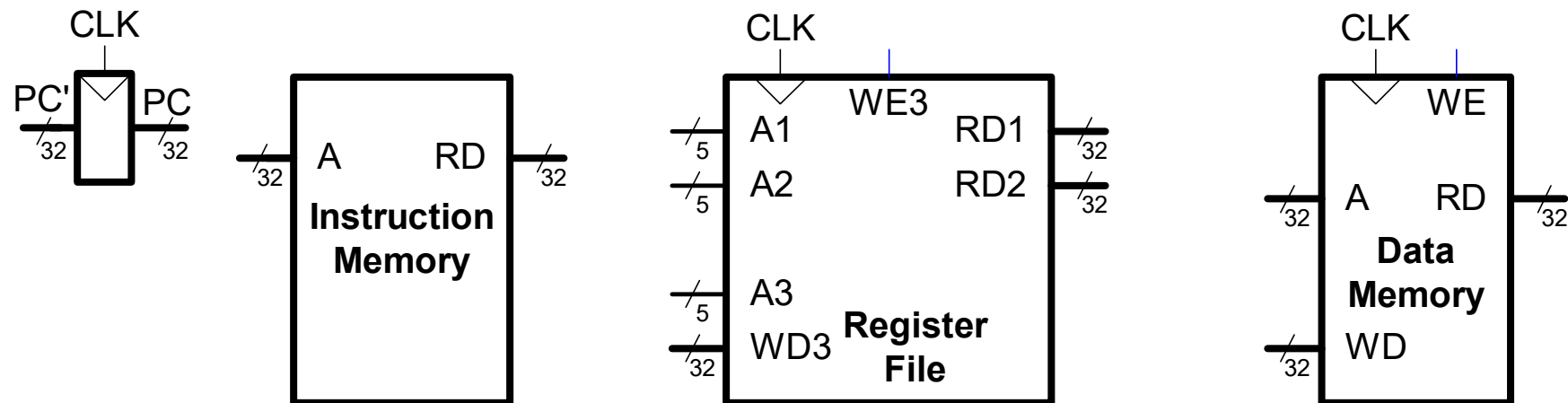

상태 요소들 == 메모리 요소들




Single-Cycle MIPS Processor

- Datapath (데이터가 계산되는 흐름)
- Control (제어신호를 생성하는 흐름)




Single-Cycle Datapath

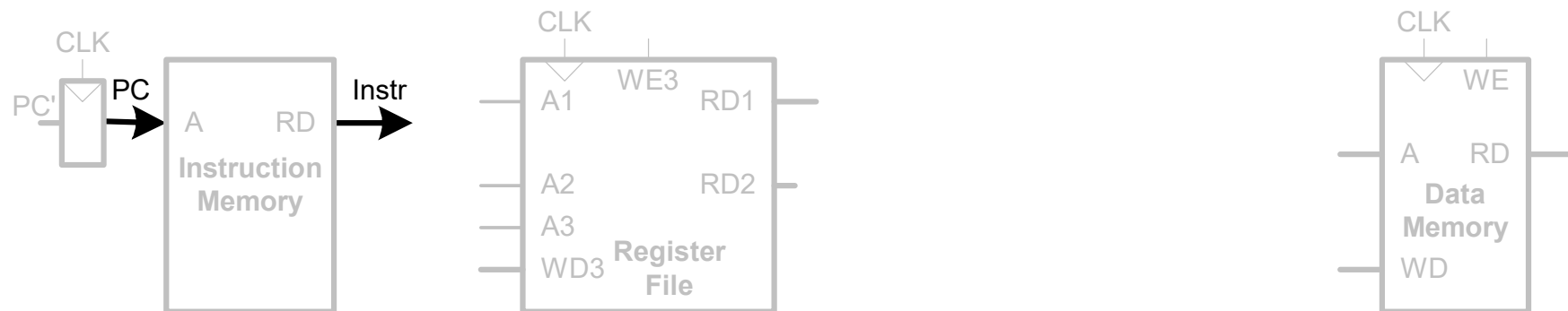- First consider executing **lw**
우선, **lw** 명령어의 실행을 고려해 봅시다!
- **STEP 1: Fetch instruction** (명령어 가져오기)




Single-Cycle Datapath

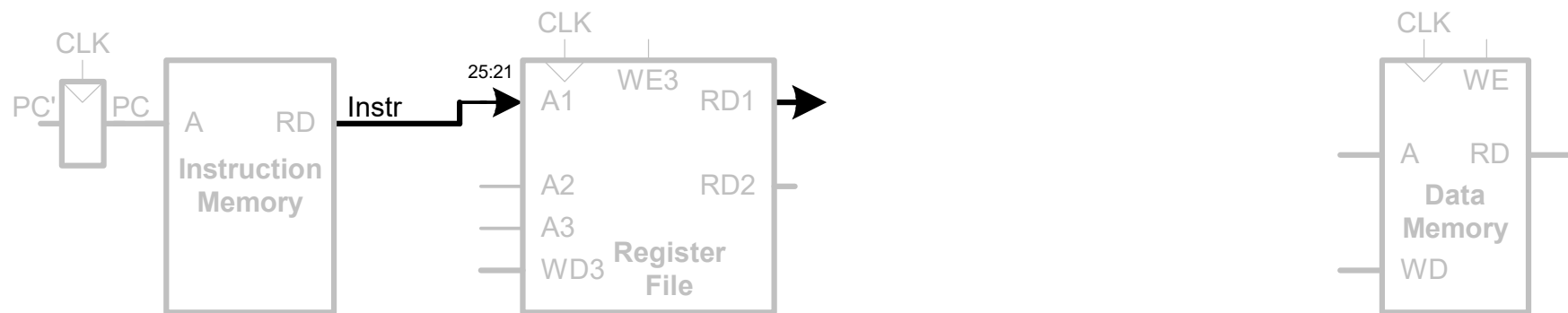- **STEP 2:** Read source operands from register file
레지스터 파일로 부터 소스 오퍼랜드 읽어오기!




I-Type

 

Single-Cycle Datapath


- **STEP 3:** Sign-extend the immediate

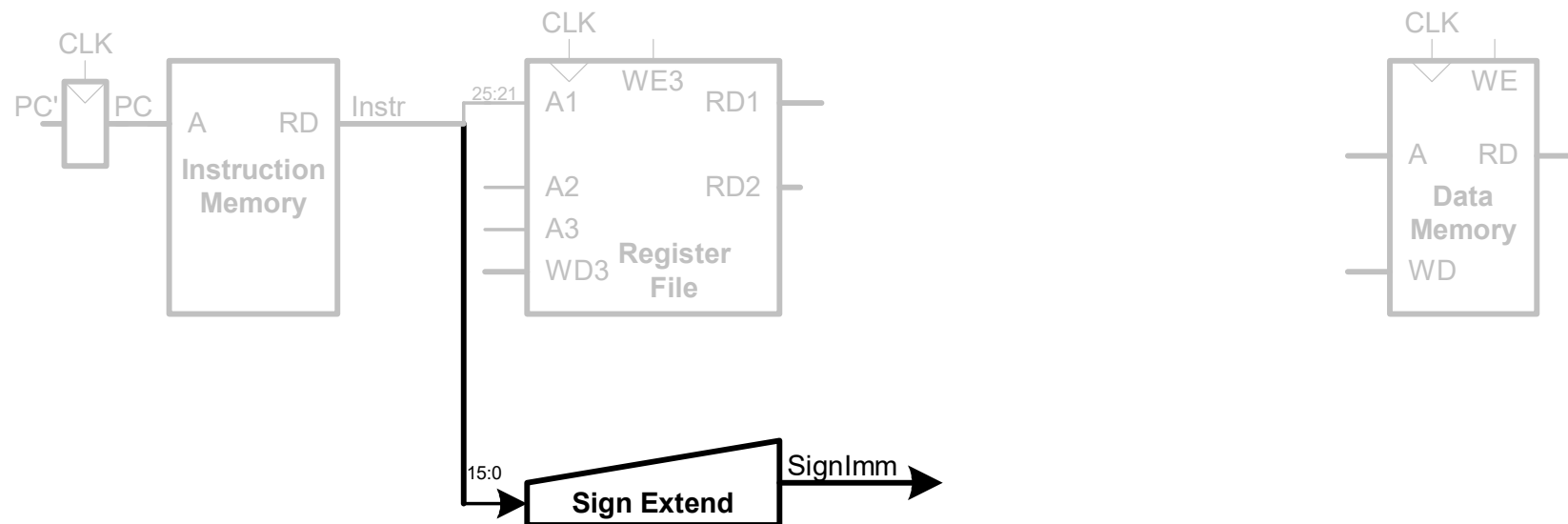

Single-Cycle Datapath

- **STEP 4:** Compute the memory address


메모리 주소 계산하기

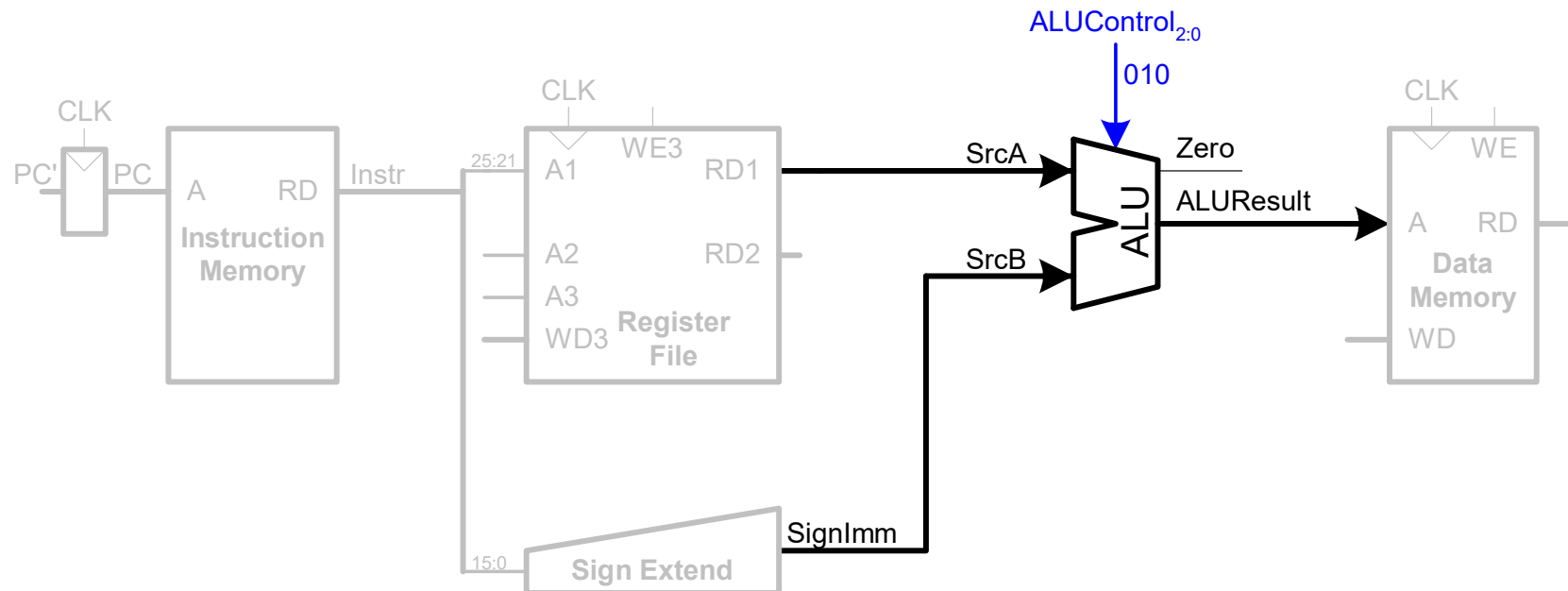

Single-Cycle Datapath

- **STEP 5:** Read data from memory and write it back to register file


메모리로부터 데이터 읽고 그 데이터를 레지스터 파일에 쓰기!

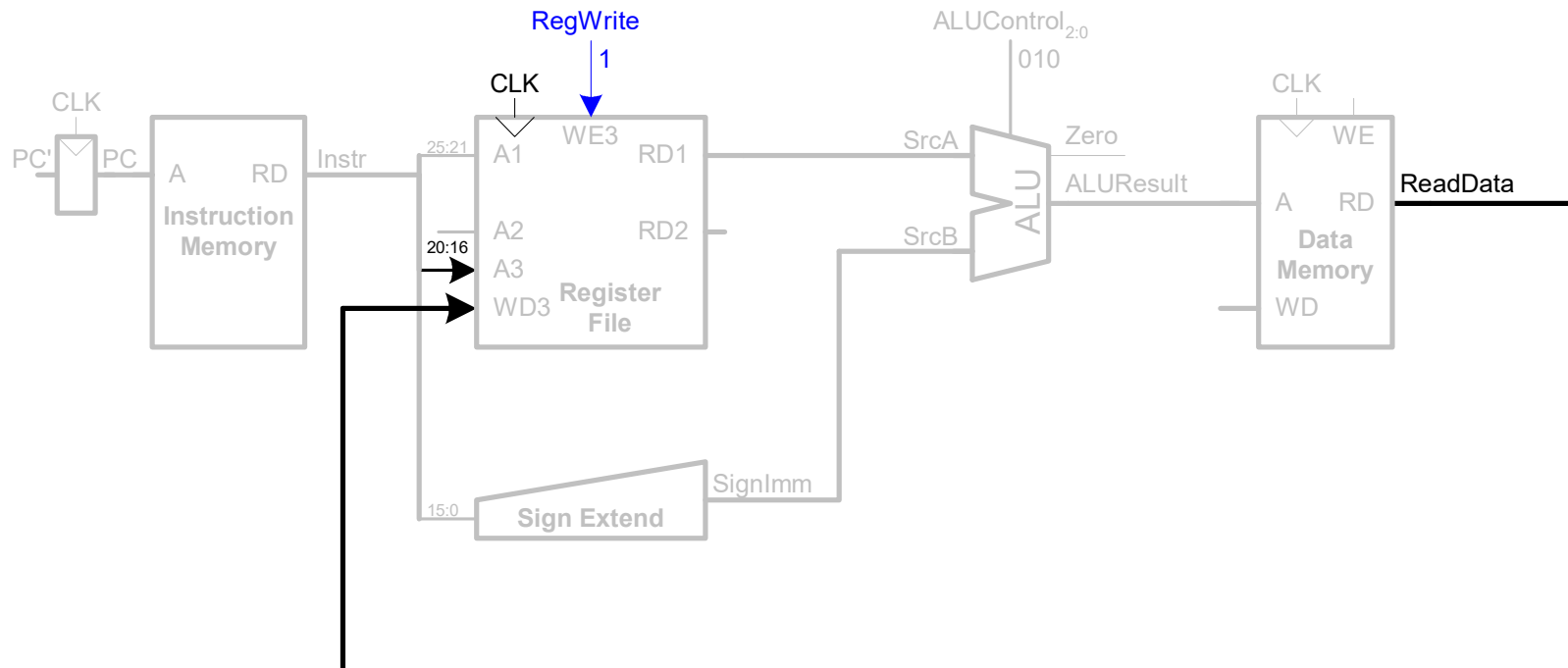

Single-Cycle Datapath


- **STEP 6:** Determine the address of the next instruction

다음 명령어의 주소를 결정하기

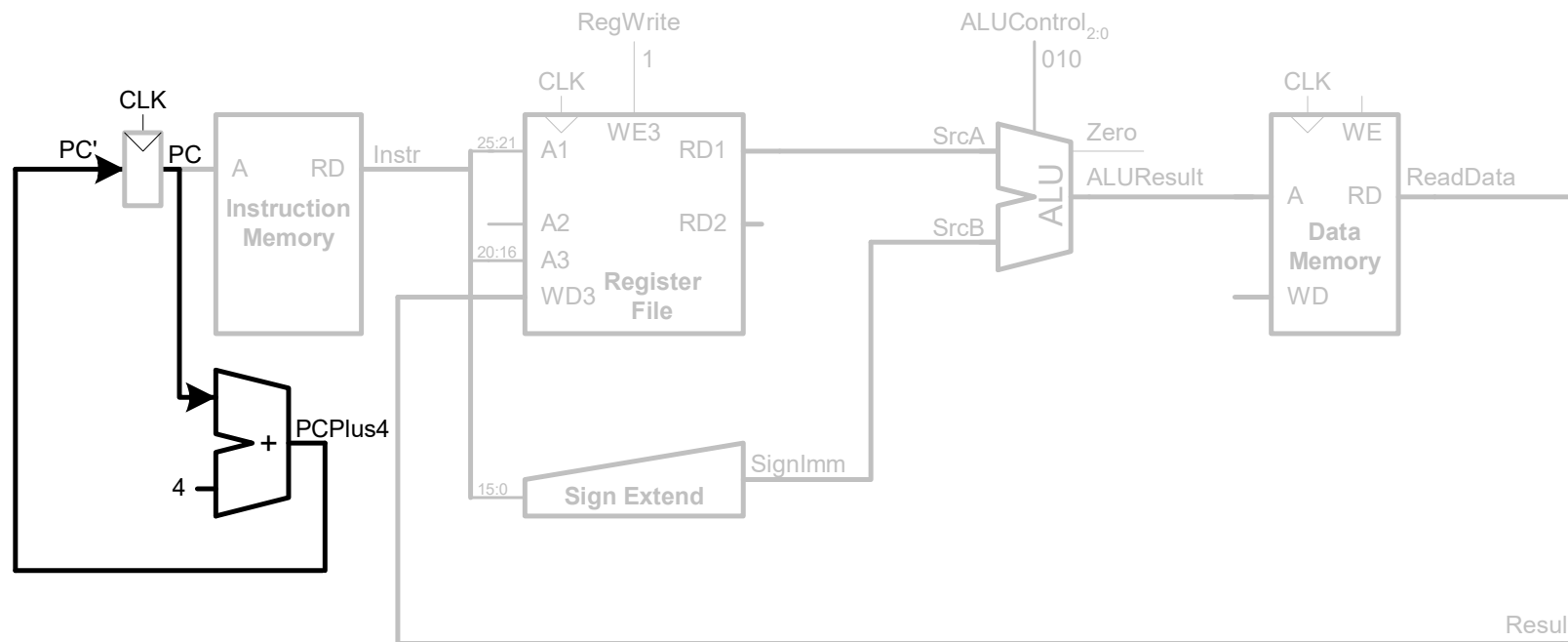


Single-Cycle Datapath

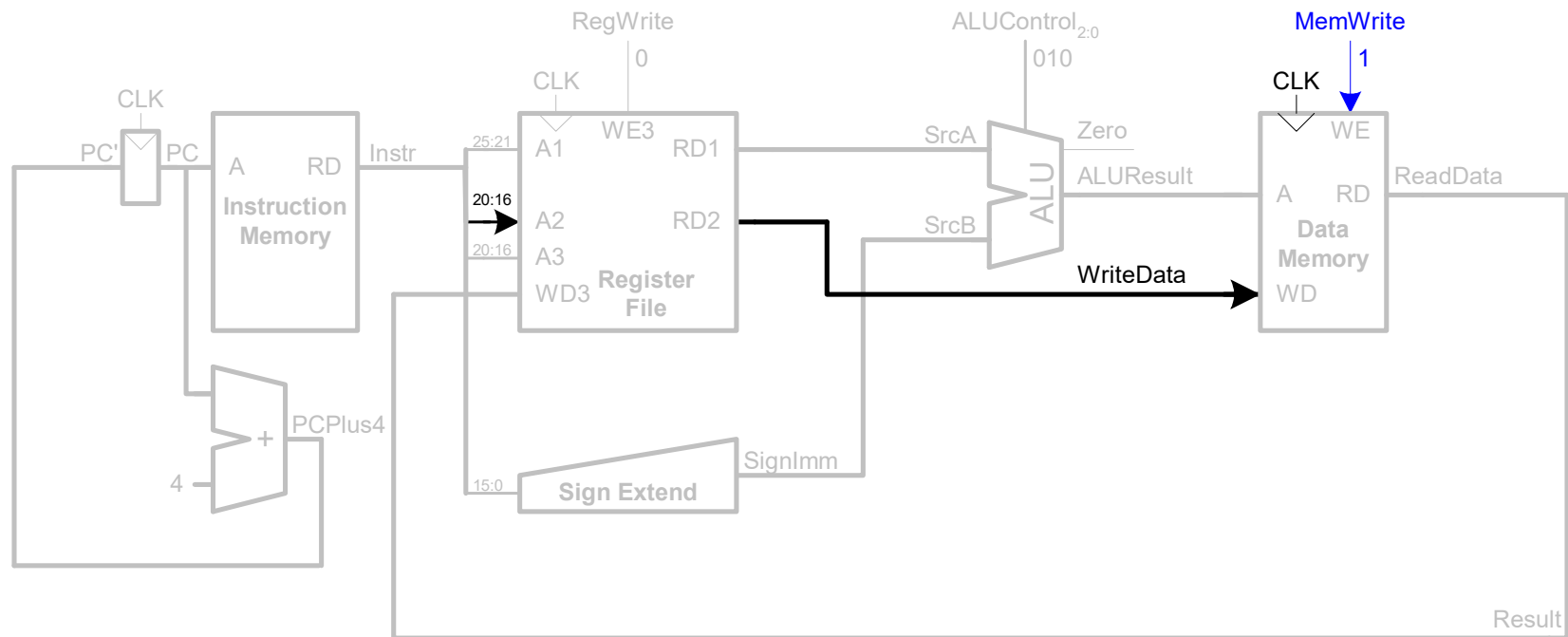- Consider **SW**
- Need to write data to memory



Single-Cycle Datapath

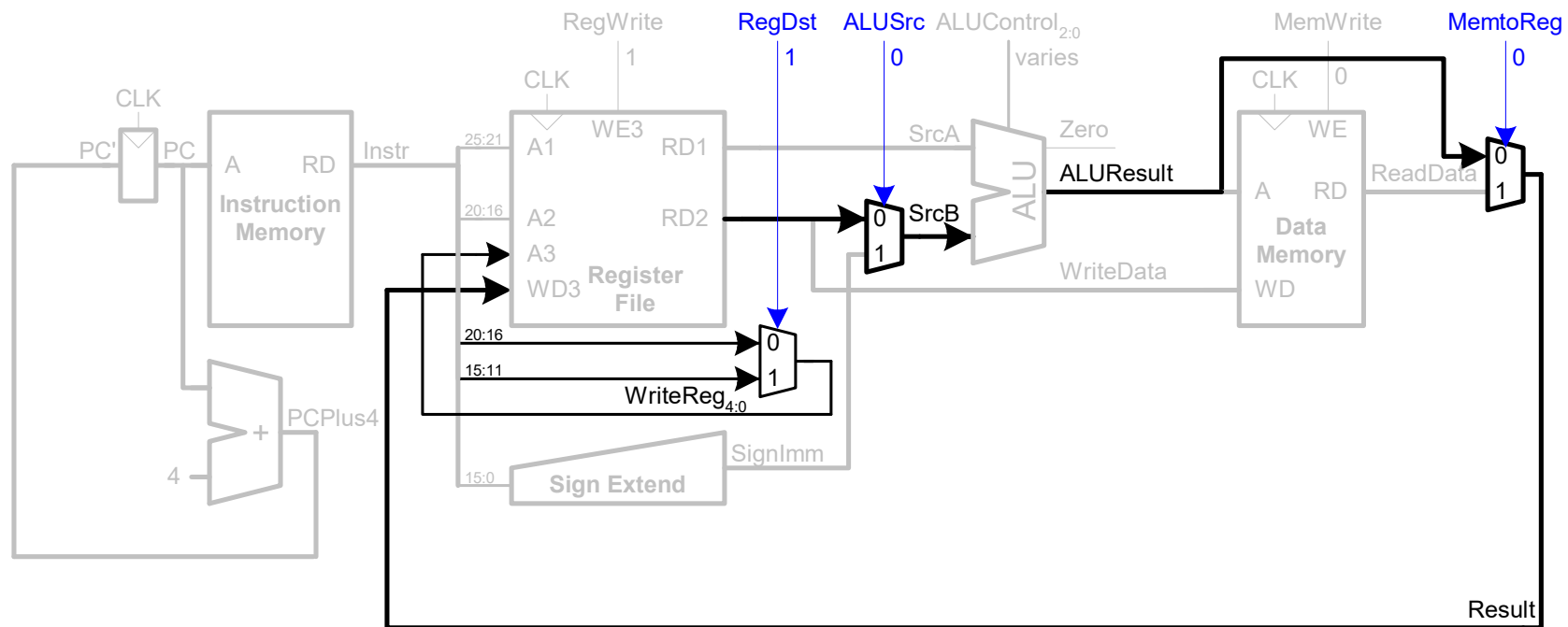- Consider **R-type** instructions: **add, sub, and, or**
- Write *ALUResult* to register file
- Writing to *rd* field of instruction (instead of *rt*)




R-Type


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-Cycle Datapath

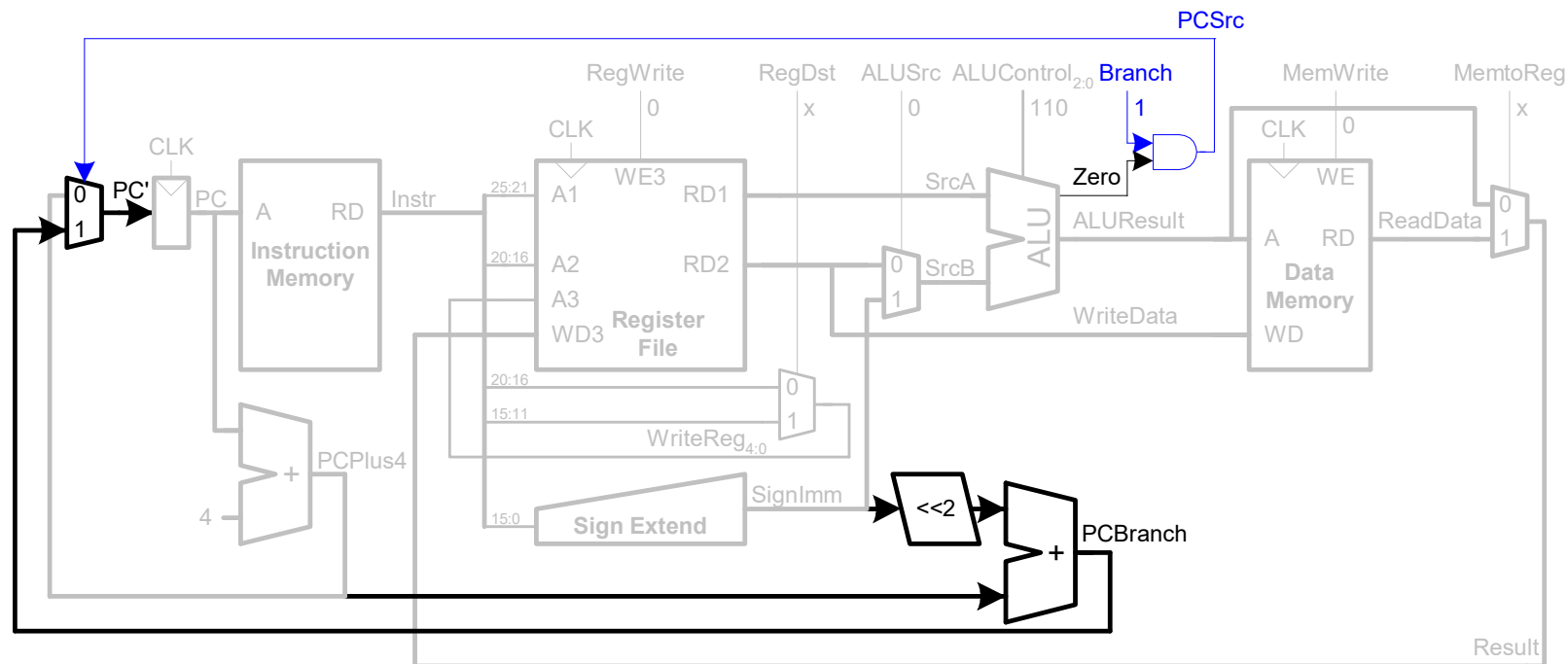
- Consider branch instruction: **beq**
- Determine whether register values are equal
- Calculate branch target address (BTA) from sign-extended immediate and PC+4




Single-Cycle Datapath Example: or

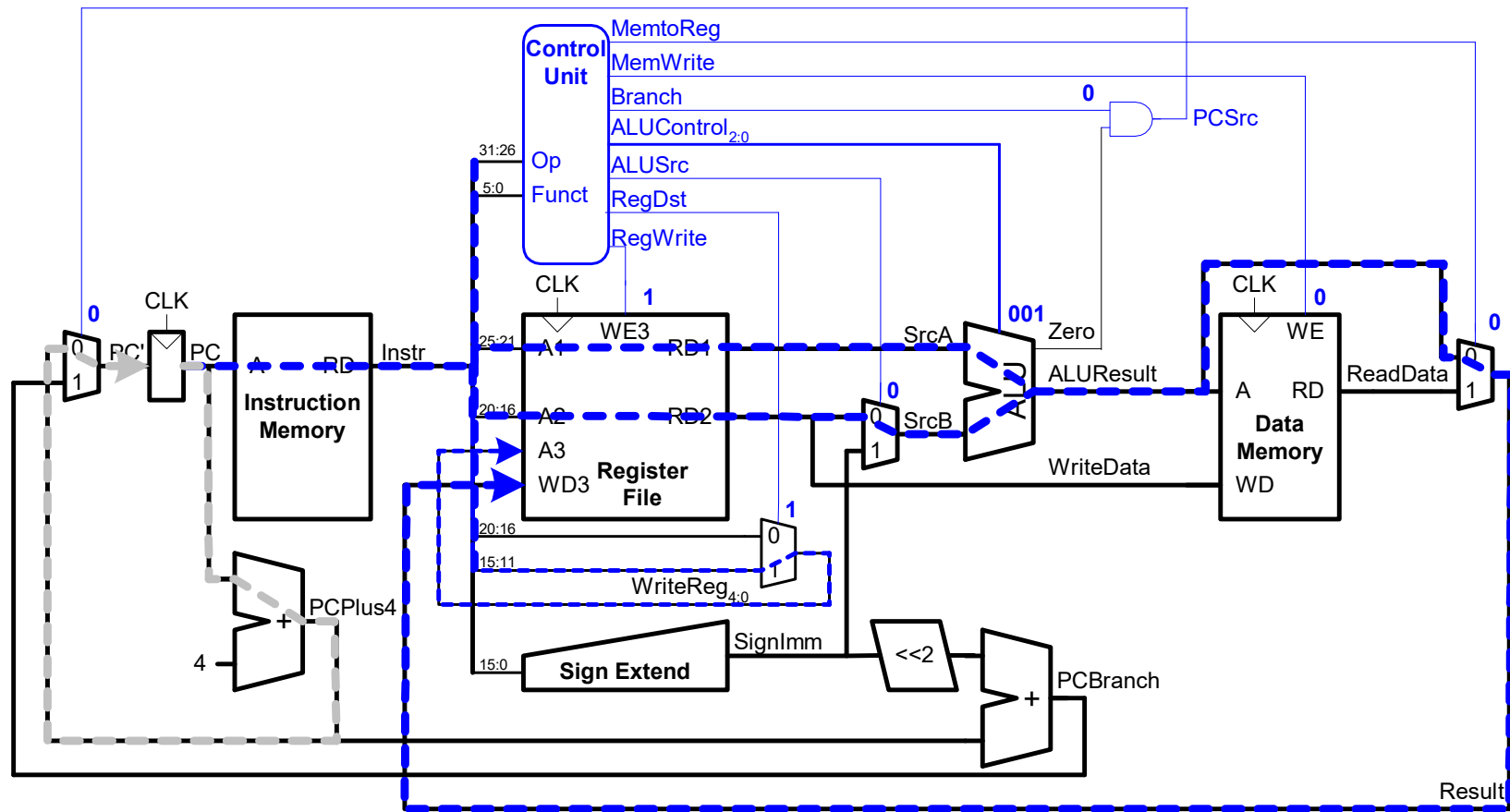


Single-Cycle Datapath: sw

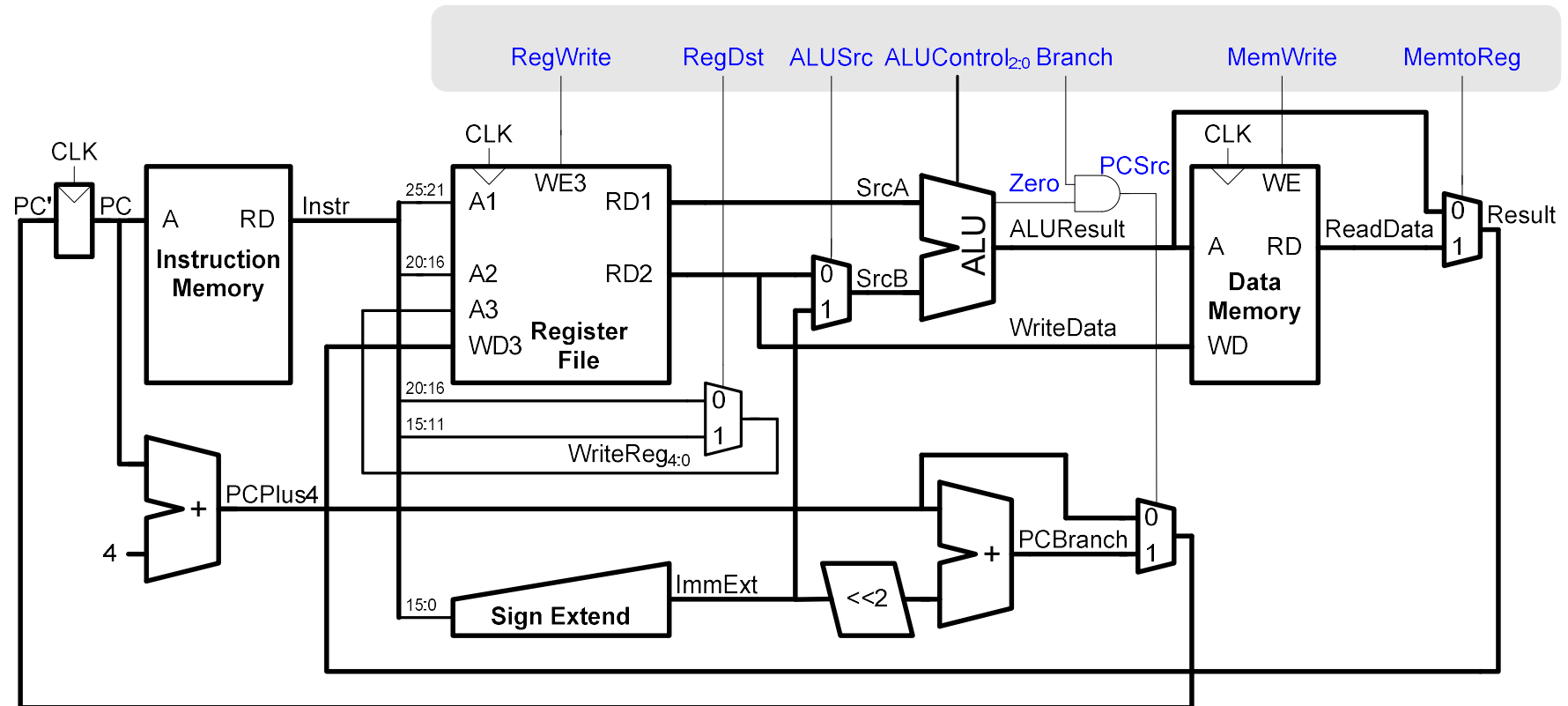


Single-Cycle Control

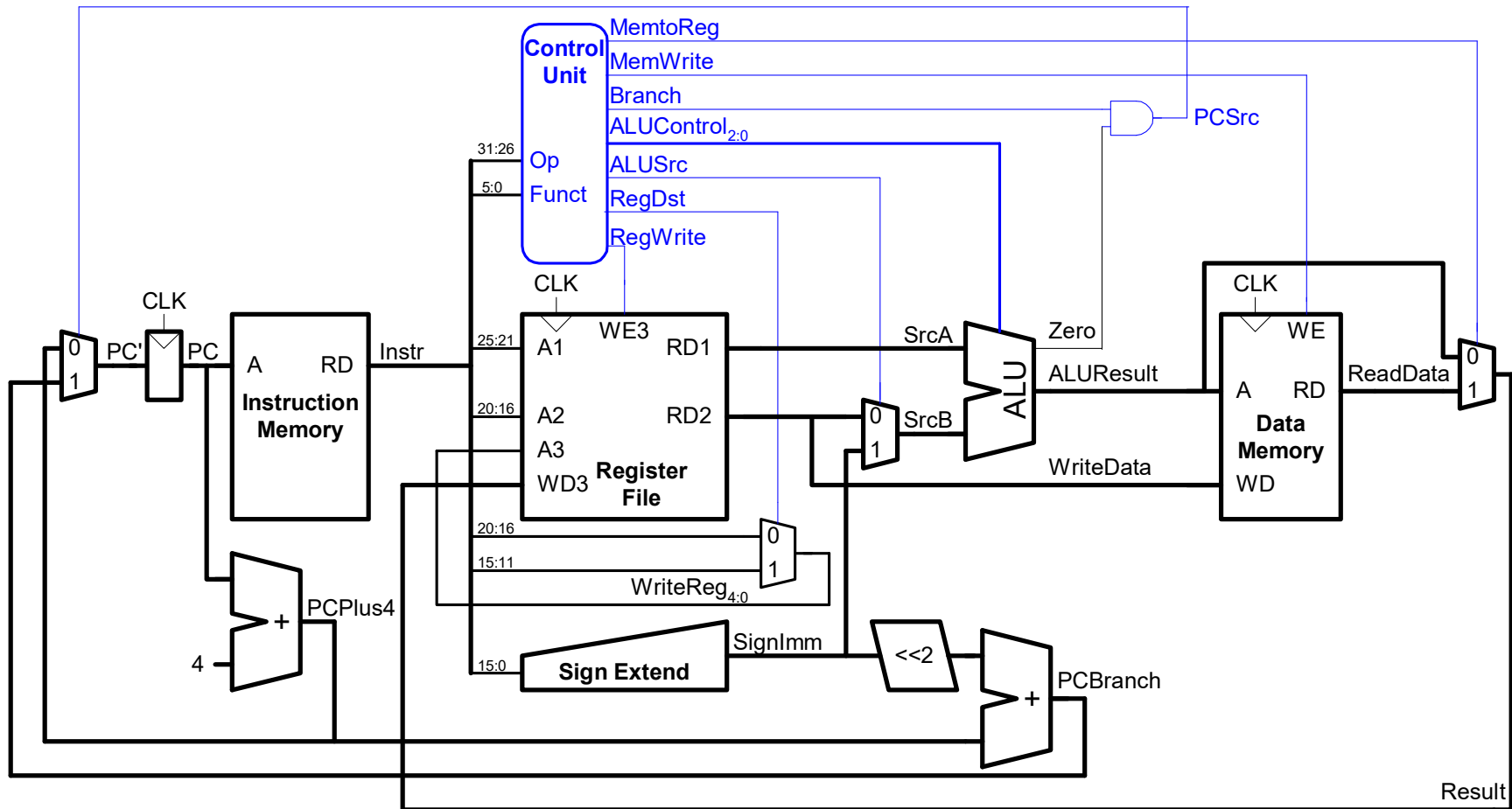

Control Unit

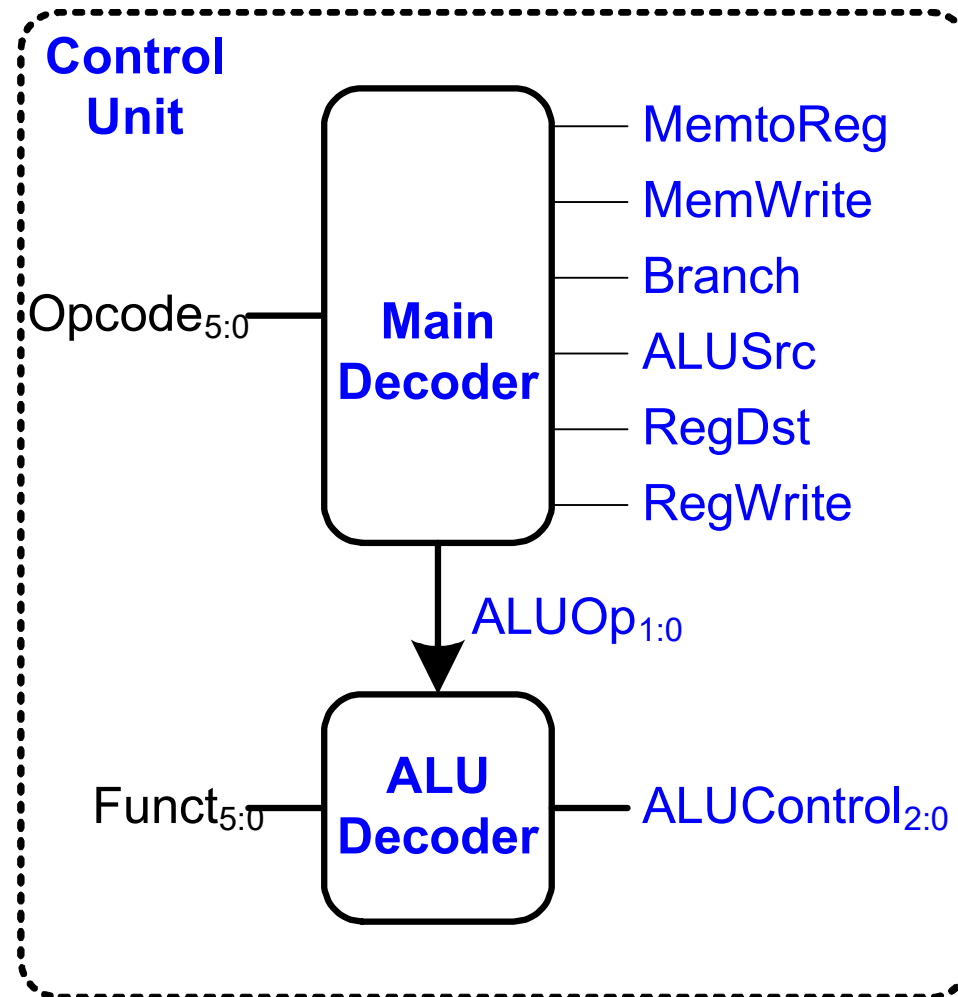


Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
0 11	not used
100	$A \& B$
101	$A \sim B$
110	$A - B$
1 11	SLT



Review: ALU

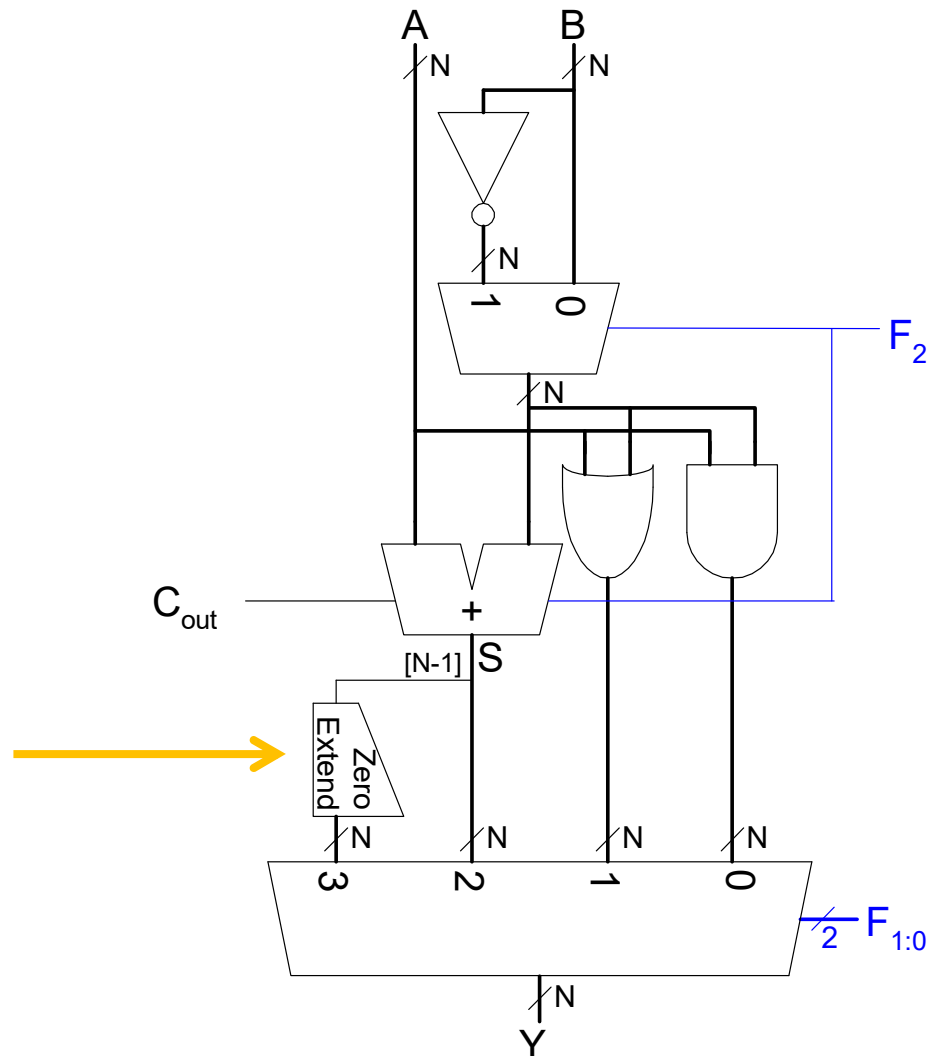

Inverting or not ?



Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used


ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01



Extended Functionality: addi

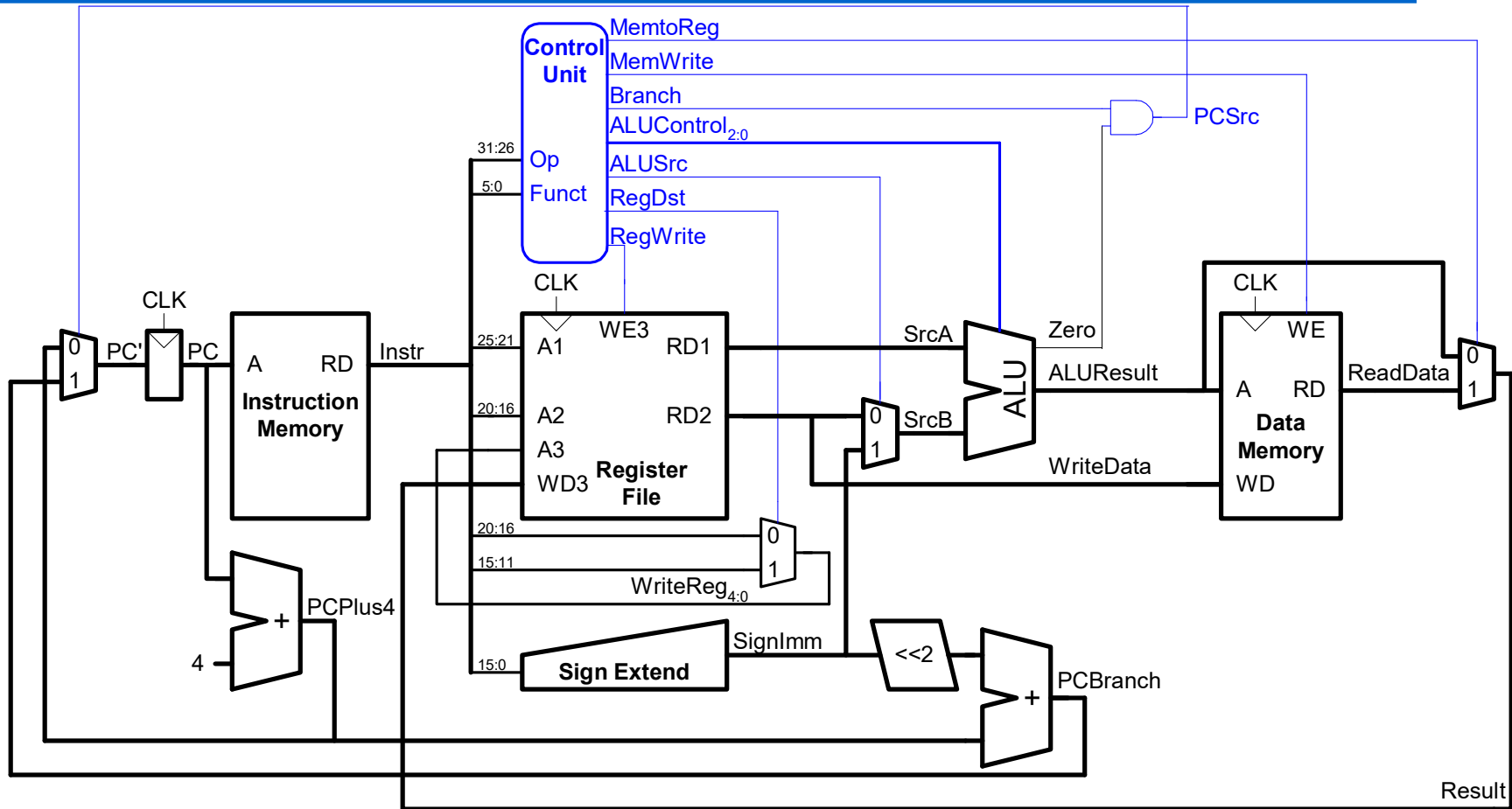


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Control Unit: Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00



Extended Functionality: j

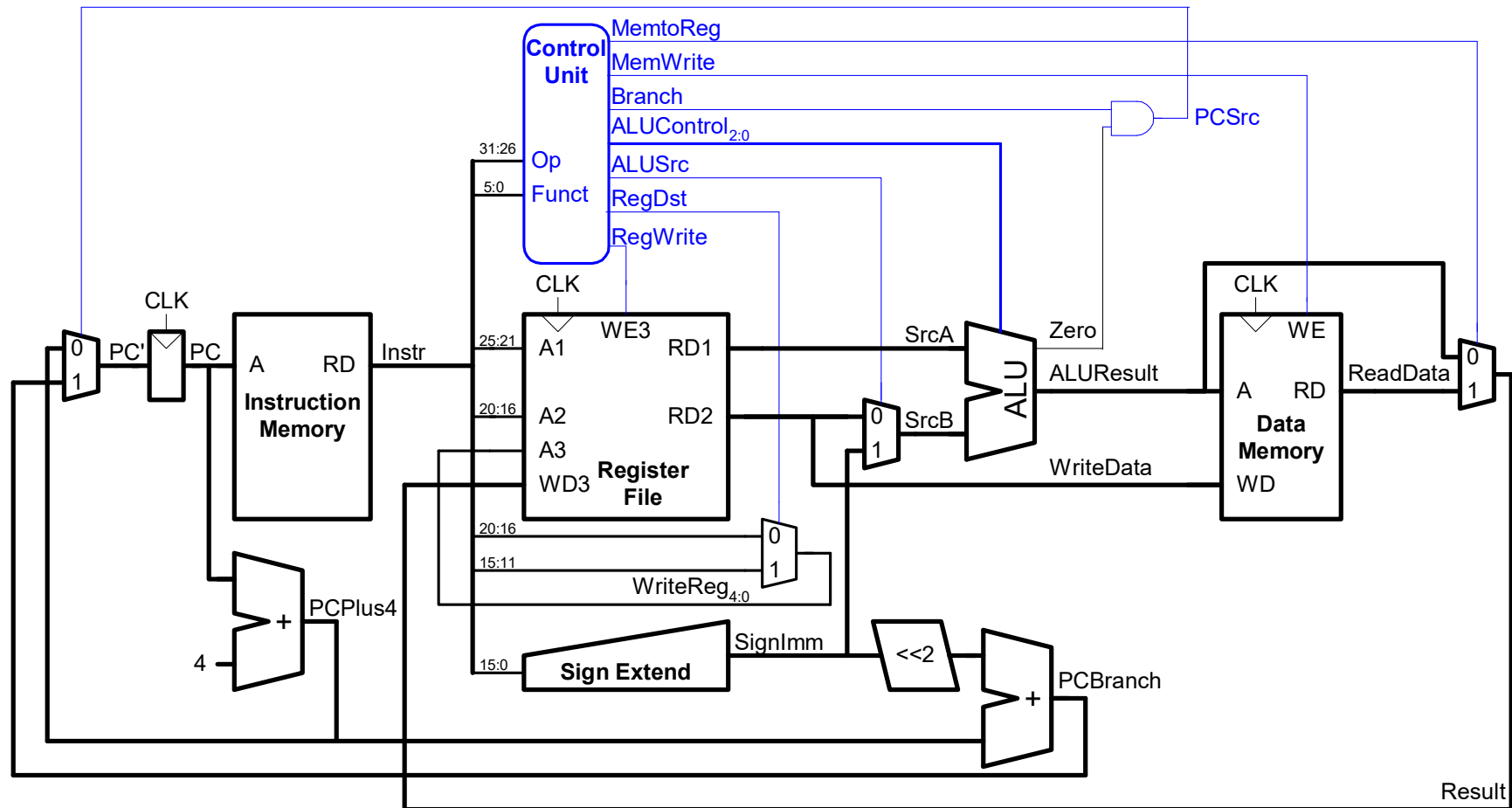

Extended Functionality: j

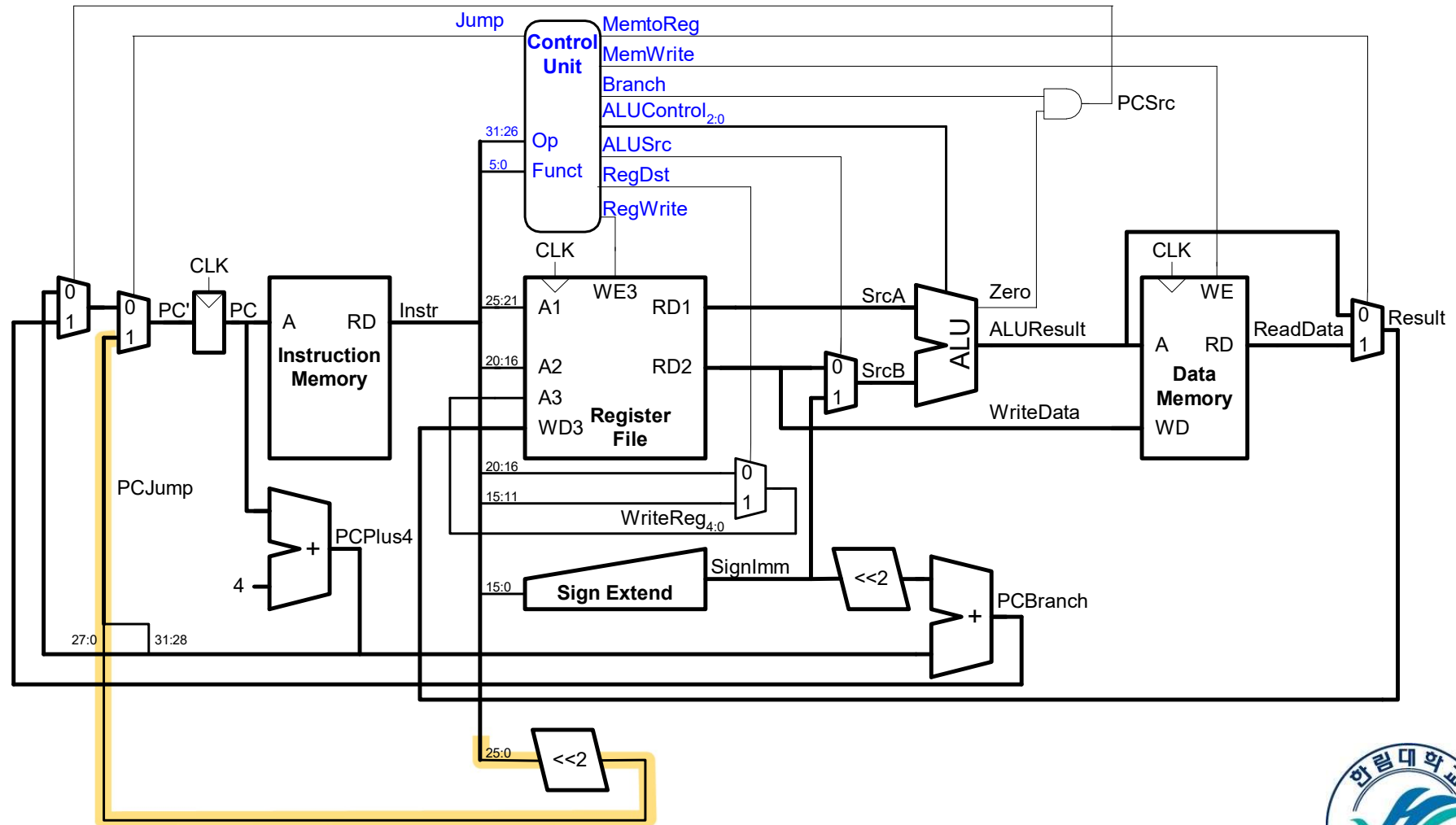


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
addi	001000	1	0	1	0	0	0	00	0
j	000100	0	X	X	X	0	X	XX	1




Single-Cycle Performance

How fast is the single-cycle processor?

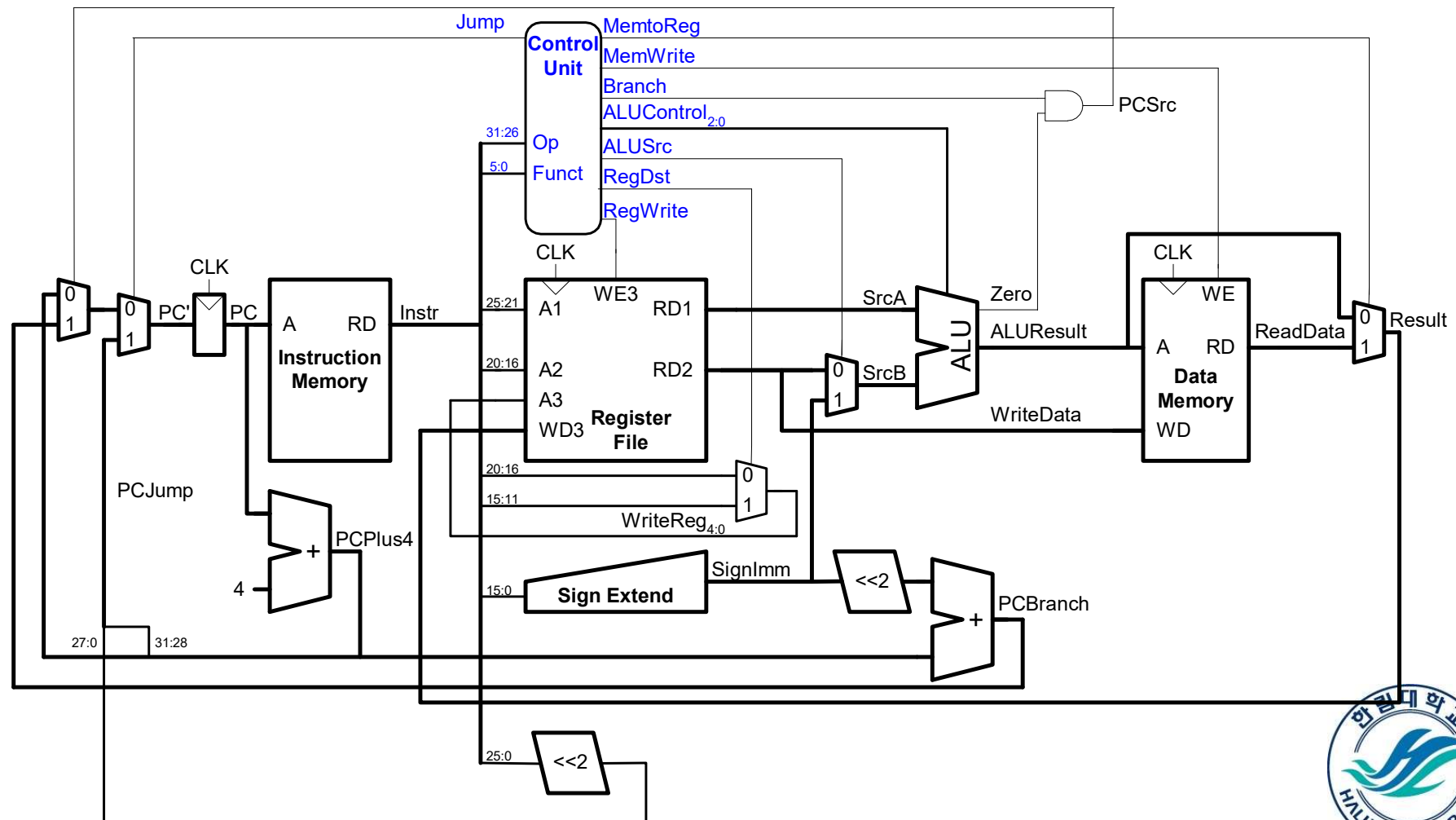

Single-Cycle Performance

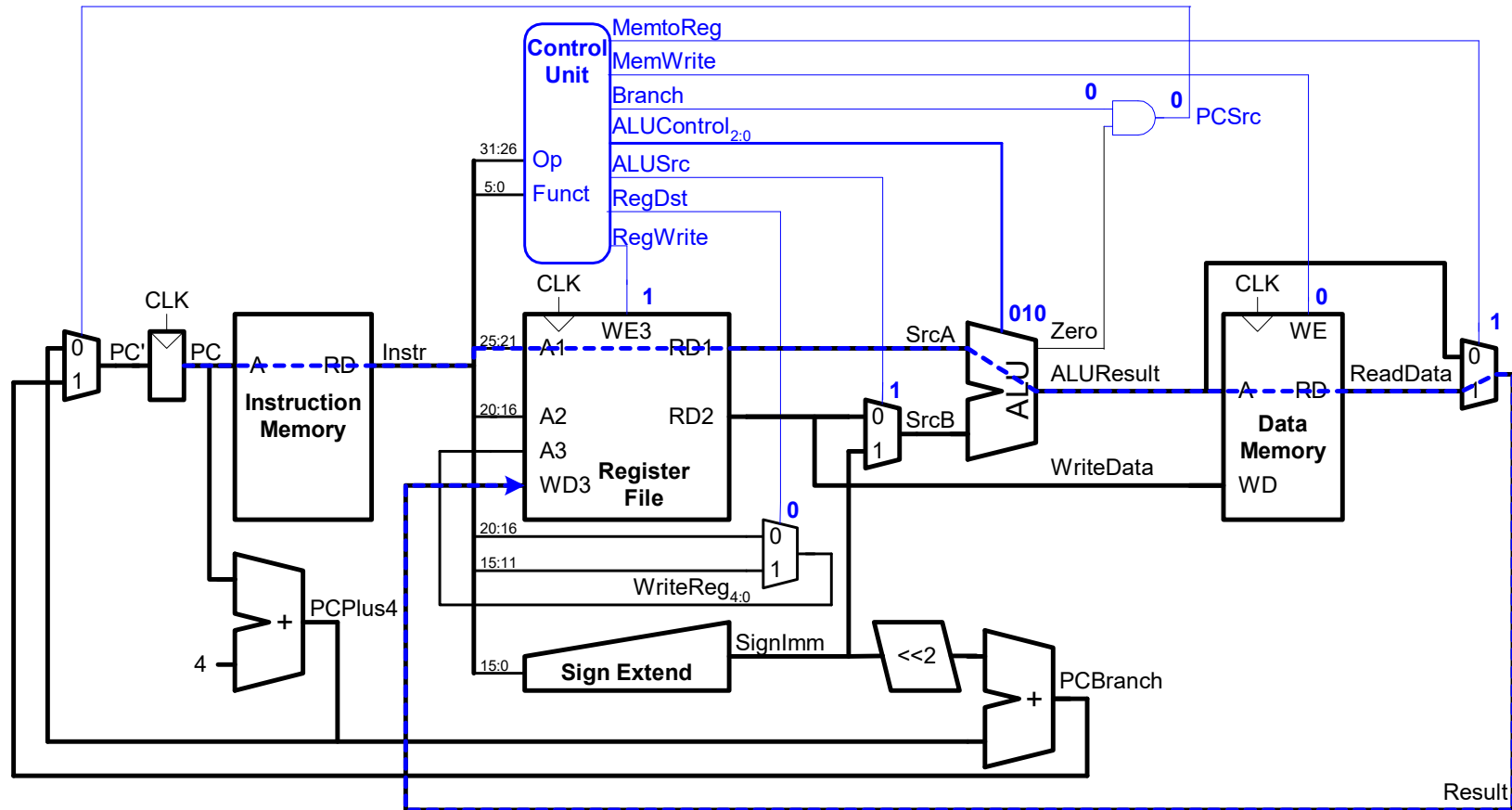- Clock cycle time is limited by the critical path (1w)



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext}) + t_{mux} + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most implementations, limiting paths are: memory, ALU, register file. Thus,

$$T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + 2t_{mux} + t_{ALU} + t_{RFsetup}$$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + 2t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 2(25) + 200 + 20] \text{ ps} \\&= 950 \text{ ps}\end{aligned}$$



Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle}) \\ &= (100 \times 10^9)(1)(950 \times 10^{-12} \text{ s}) \\ &= 95 \text{ seconds}\end{aligned}$$

